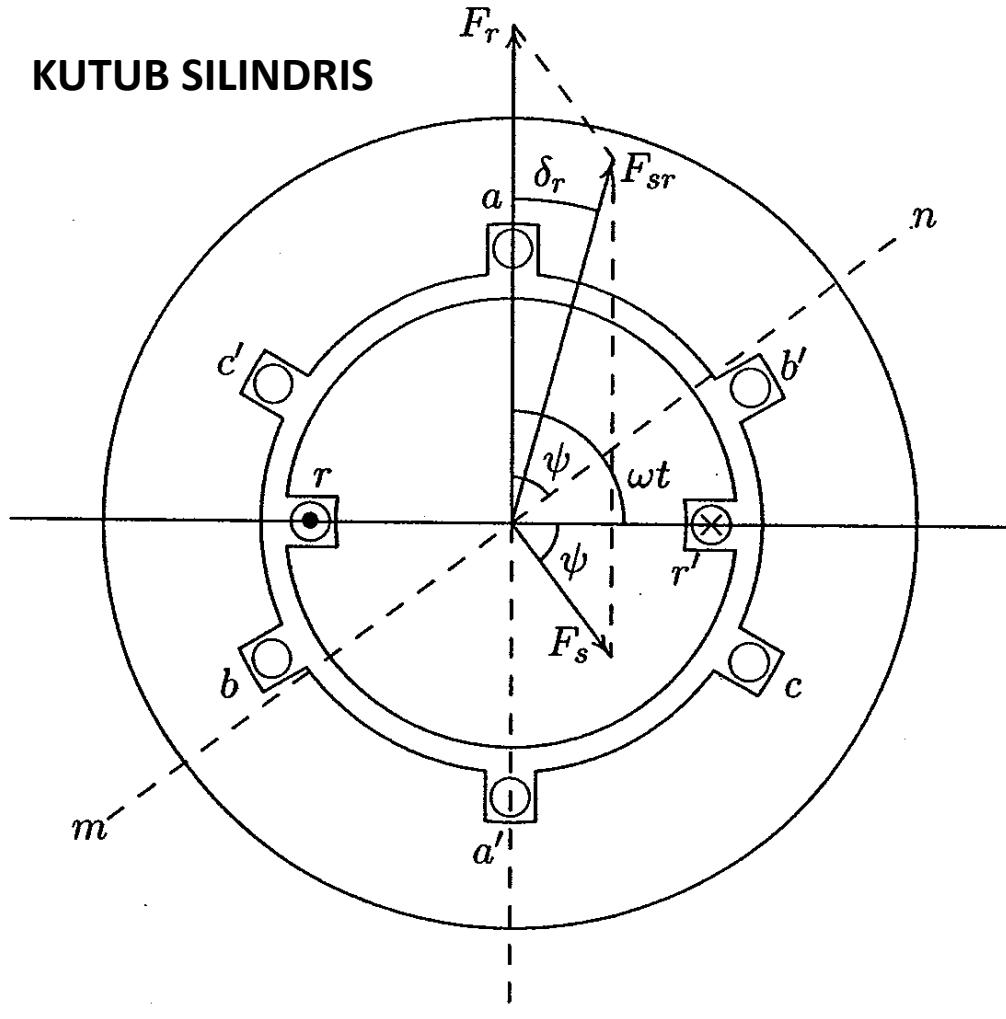


# MODEL RANGKAIAN

# MODEL RANGKAIAN GENERATOR SINKRON

# KUTUB SILINDRIS




$$E = 4.44 f N \phi$$

$$E = 4.44K_w f N \phi$$

$$f = \frac{P}{2} \frac{n}{60}$$

### **FIGURE 3.1**

## Elementary two-pole three-phase synchronous generator.

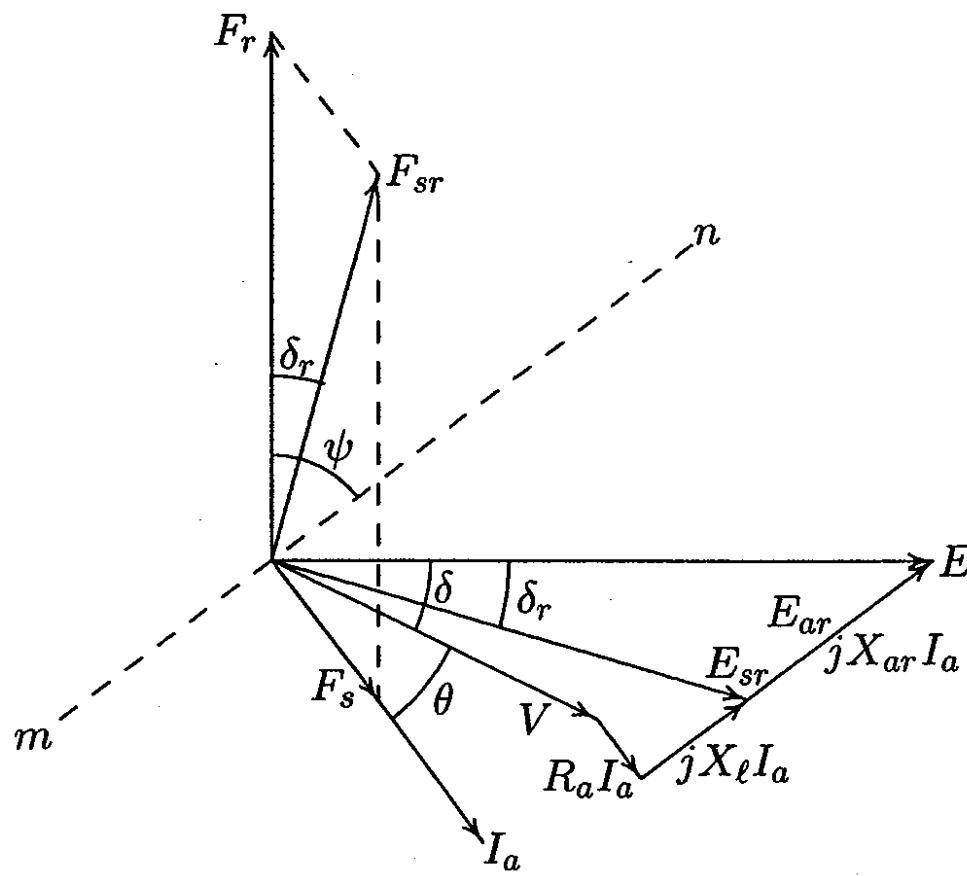

**FIGURE 3.2**

Combined phasor/vector diagram for one phase of a cylindrical rotor generator.


$$E = E_{sr} + jX_{ar}I_a$$

$$E = V + [R_a + j(X_\ell + X_{ar})]I_a$$

$$E = V + [R_a + jX_s]I_a$$

$$X_s = (X_\ell + X_{ar})$$


**Xs = Reaktansi sinkron**

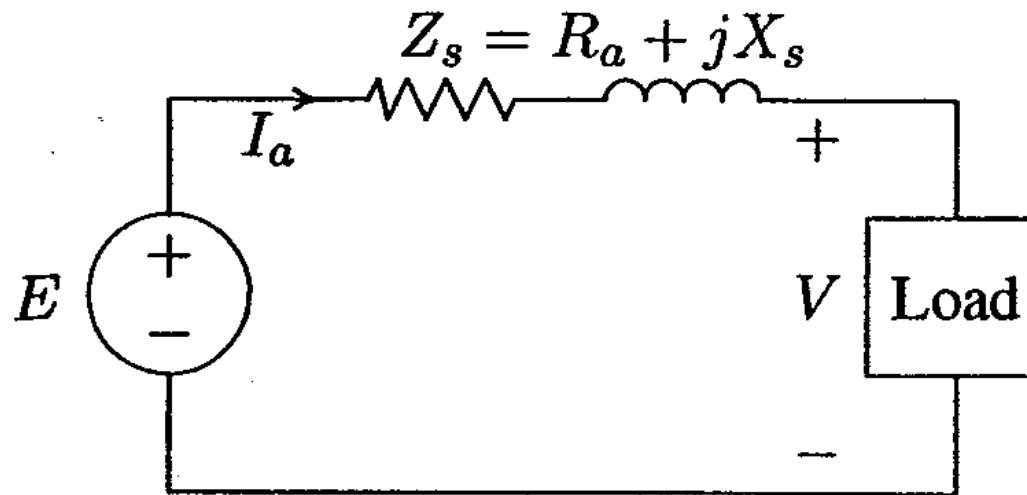

**FIGURE 3.3**  
Synchronous machine equivalent circuit.


$R_a \ll X_s$

$$E = V + jX_s I_a$$

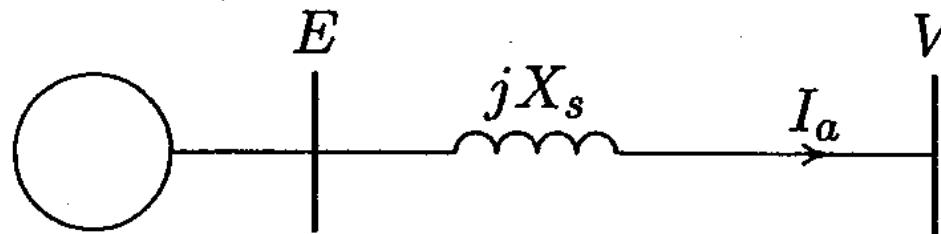

**FIGURE 3.4**  
Synchronous machine connected to an infinite bus.

# PENGATURAN EKSITASI

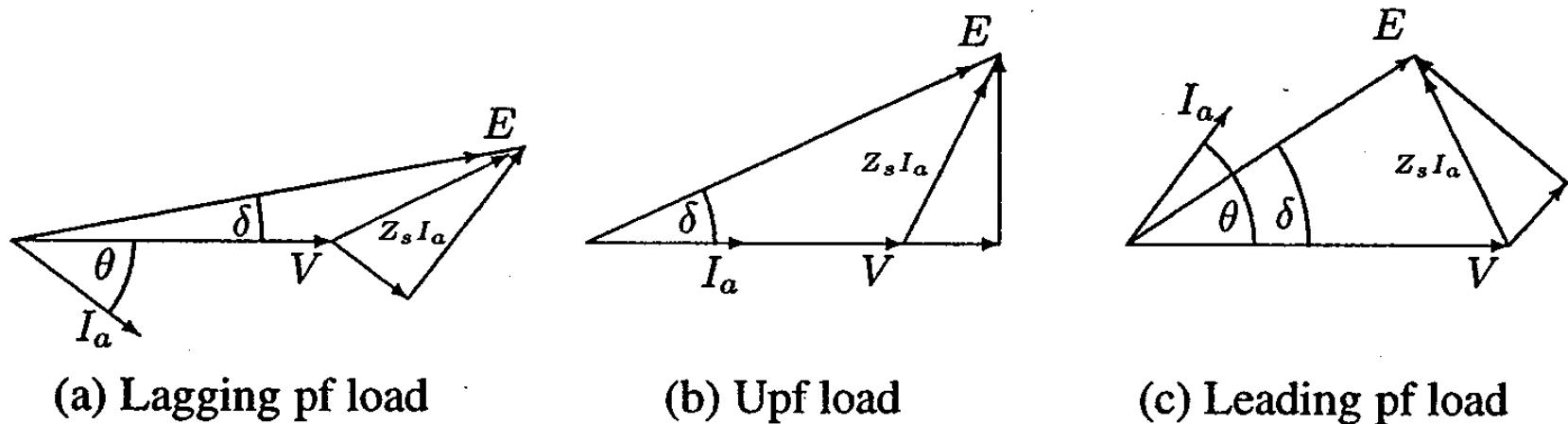

**FIGURE 3.5**  
Synchronous generator phasor diagram.

## PENGATUR TEGANGAN/VOLTAGE REGULATION

$$VR = \frac{|V_{nl}| - |V_{rated}|}{|V_{rated}|} \times 100 = \frac{|E| - |V_{rated}|}{|V_{rated}|} \times 100$$

# SALIENT-POLE SYNCHRONOUS GENERATORS


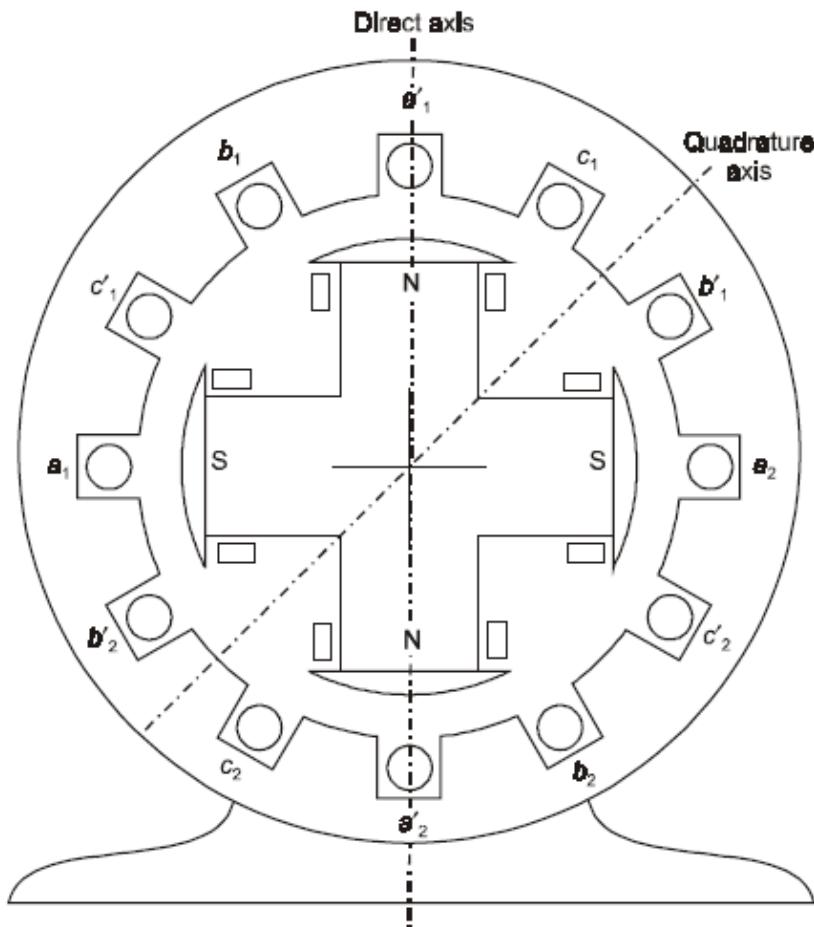


Fig. 4.5: Schematic representation of a salient pole synchronous generator (four poles).

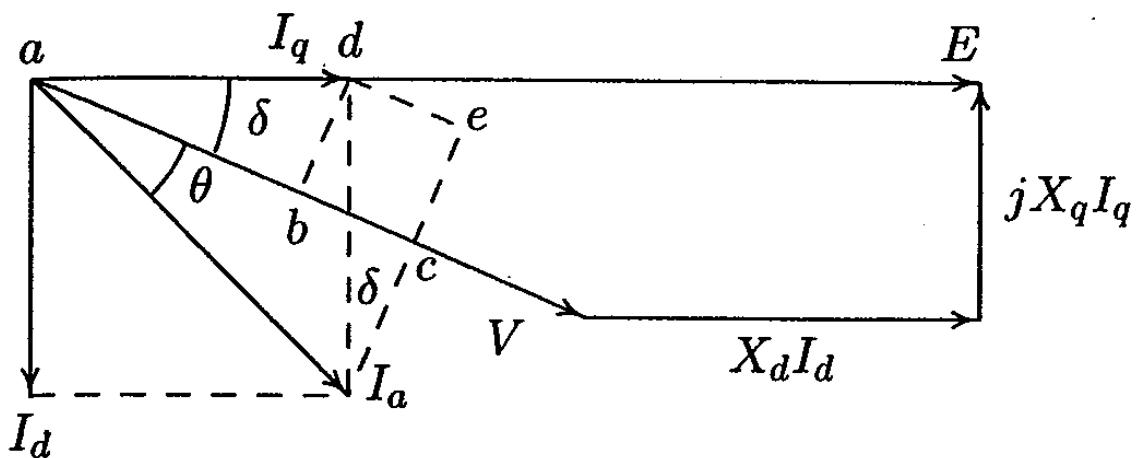

**FIGURE 3.8**

Phasor diagram for a salient-pole generator.

$$|E| = |V| \cos \delta + X_d I_d$$

The three-phase real power at the generator terminal is

$$P = 3|V||I_a| \cos \theta$$


$$I_d = \frac{|E| - |V| \cos \delta}{X_d}$$

$$I_q = \frac{|V| \sin \delta}{X_q}$$

$$P = 3|V|(I_q \cos \delta + I_d \sin \delta)$$

$$P_{3\phi} = 3 \frac{|E||V|}{X_d} \sin \delta + 3|V|^2 \frac{X_d - X_q}{2X_d X_q} \sin 2\delta$$

# MODEL TRANSFORMATOR

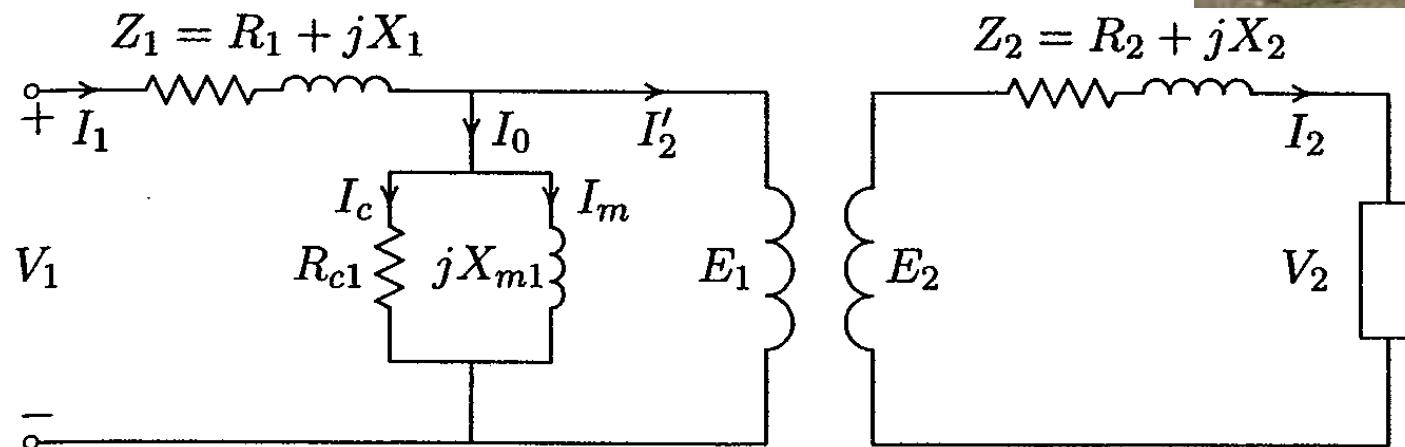


**FIGURE 3.9**  
Equivalent circuit of a transformer.

$$E_1 = 4.44 f N_1 \Phi_{max}$$


$$E_2 = 4.44 f N_2 \Phi_{max}$$

$$\frac{E_1}{E_2} = \frac{I_2}{I'_2} = \frac{N_1}{N_2}$$

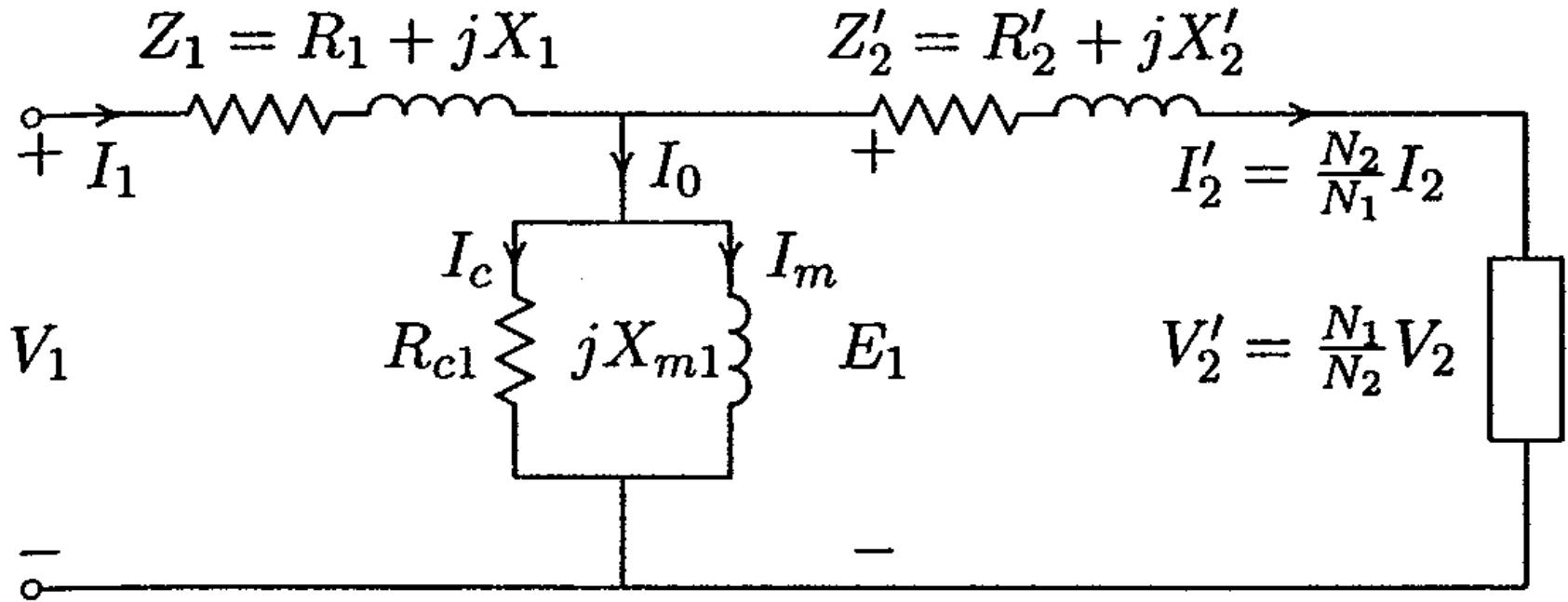

**FIGURE 3.10**

Exact equivalent circuit referred to the primary side.

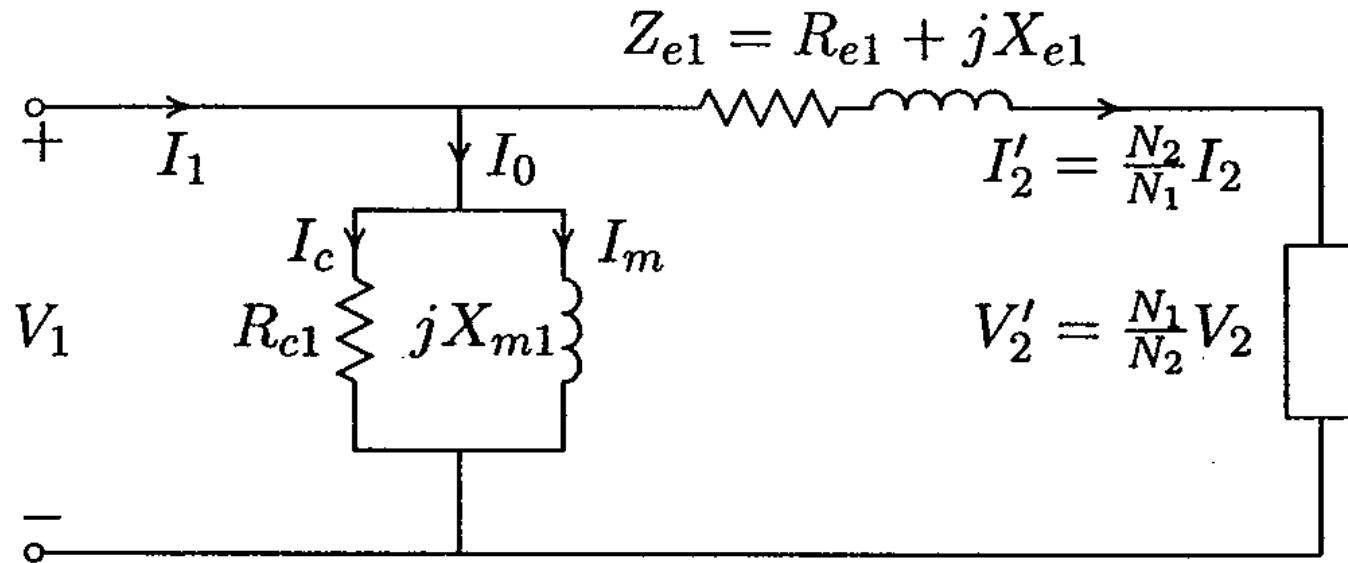


**FIGURE 3.11**

Approximate equivalent circuit referred to the primary.

$$V_1 = V'_2 + (R_{e1} + jX_{e1})I'_2$$

where

$$R_{e1} = R_1 + \left(\frac{N_1}{N_2}\right)^2 R_2 \quad X_{e1} = X_1 + \left(\frac{N_1}{N_2}\right)^2 X_2 \quad \text{and} \quad I'_2 = \frac{S_L^*}{3V_2'^*}$$

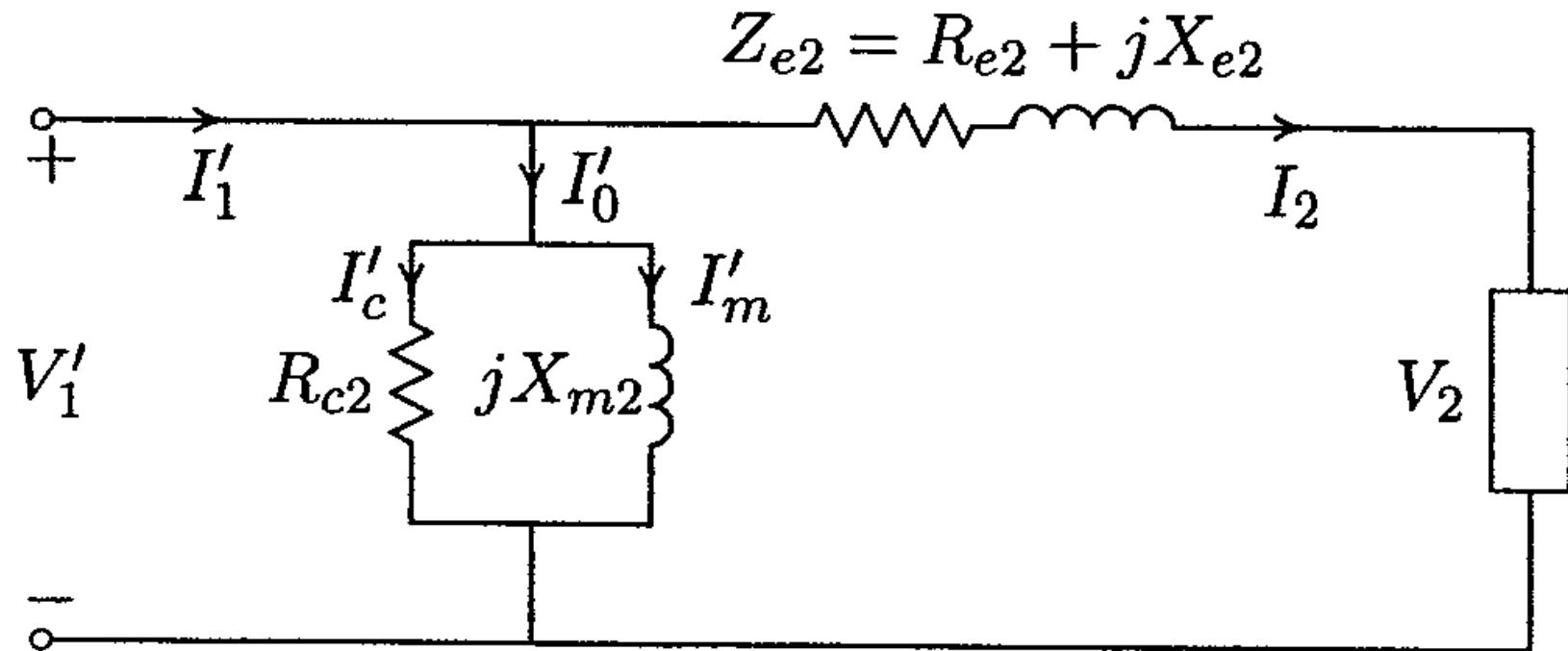


**FIGURE 3.12**

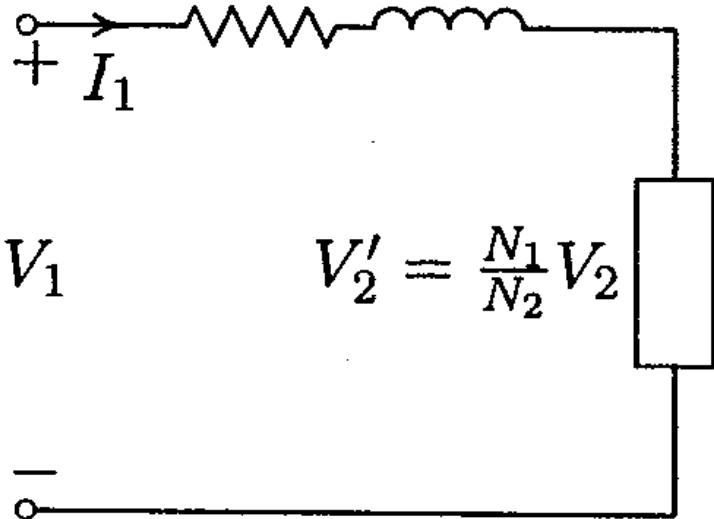Approximate equivalent circuit referred to the secondary.

$$V'_1 = V_2 + (R_{e2} + jX_{e2})I_2$$


$$Z_{e1} = R_{e1} + jX_{e1}$$



$$V'_2 = \frac{N_1}{N_2} V_2$$

$$Z_{e2} = R_{e2} + jX_{e2}$$


$$V'_1 = \frac{N_2}{N_1} V_1$$

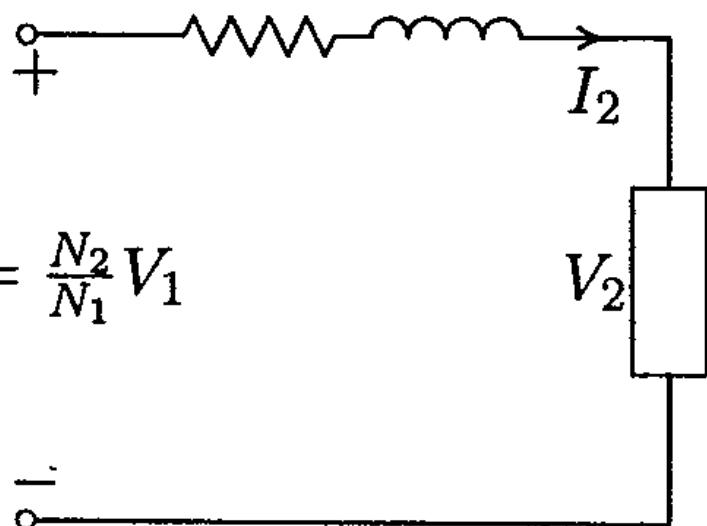


**FIGURE 3.13**

Simplified circuits referred to one side.



# HUBUNGAN TRANFORMATOR TIGA PHASA

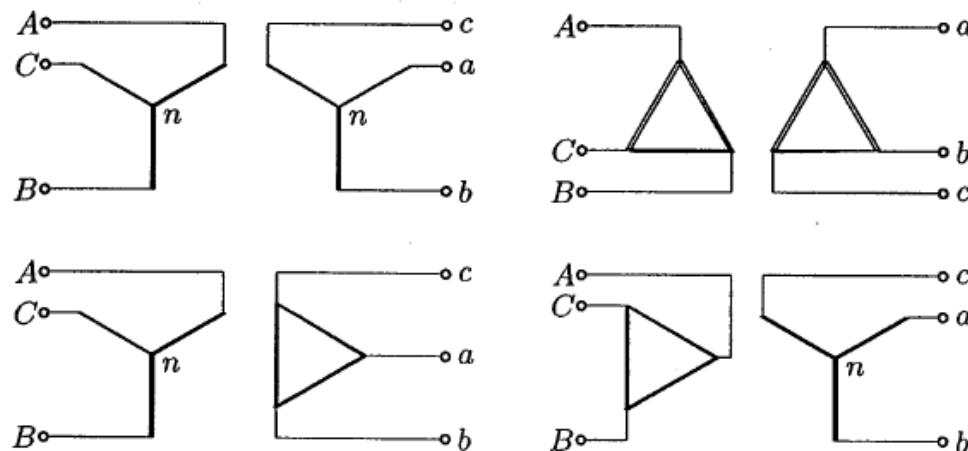

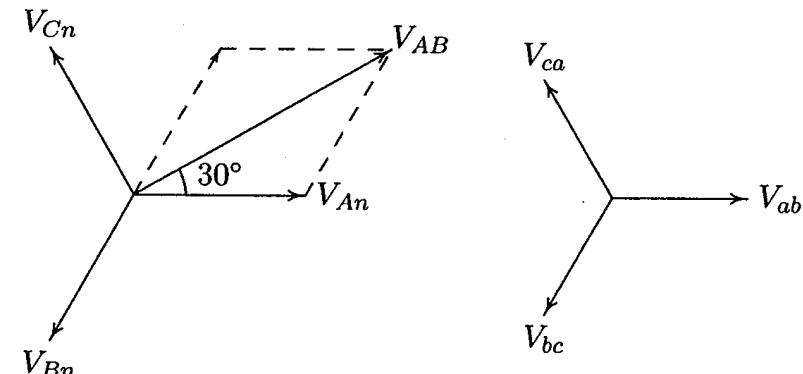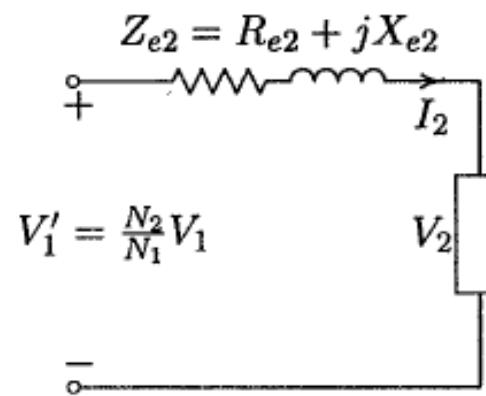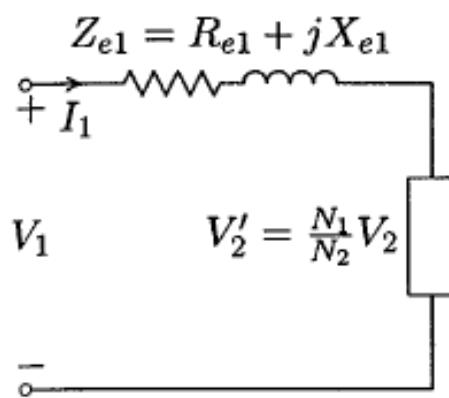**FIGURE 3.17**  
Three-phase transformer connections.


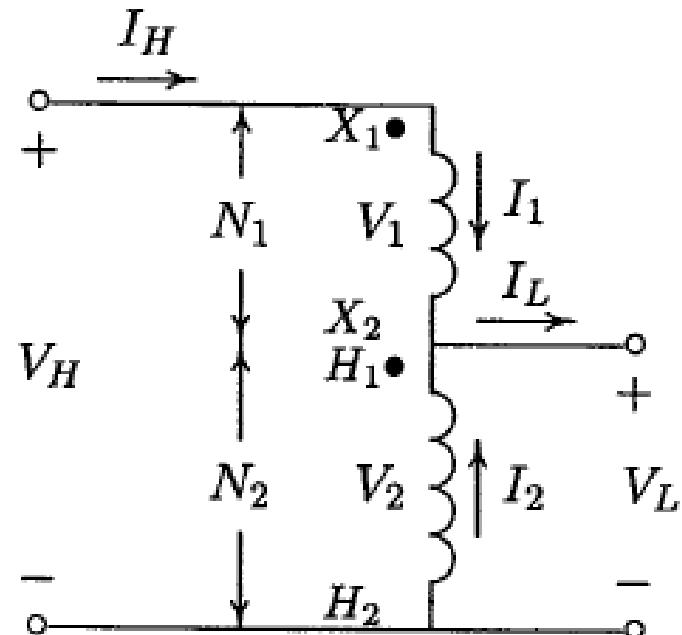


**FIGURE 3.18**  
30° phase shift in line-to-line voltages of Y-Δ connection.

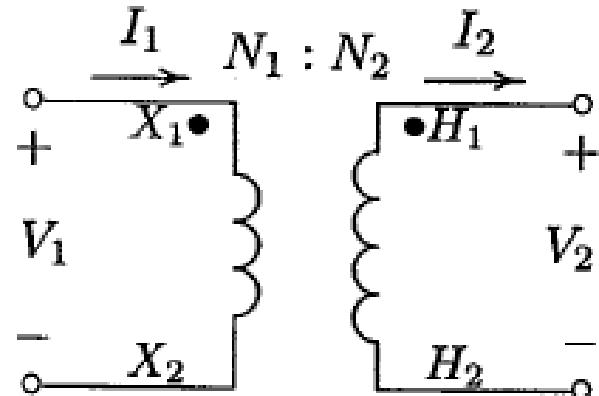

**FIGURE 3.19**  
The per phase equivalent circuit.

# AUTOTRANSFORMER



**FIGURE 3.20**

(a) Two-winding transformer, (b) reconnected as an autotransformer.

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a$$


$$V_H = V_2 + V_1$$

$$V_H = V_L + \frac{N_1}{N_2} V_L$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = a$$


$$V_H = V_2 + \frac{N_1}{N_2} V_2$$

$$= (1 + a)V_L$$

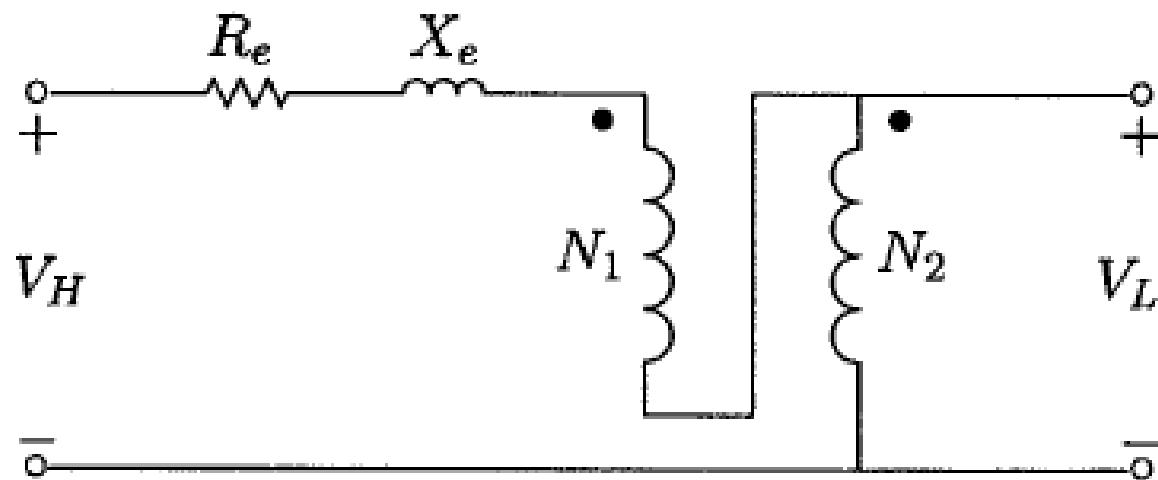

**FIGURE 3.22**  
Autotransformer equivalent circuit.

# TRANSFORMATOR TIGA BELITAN

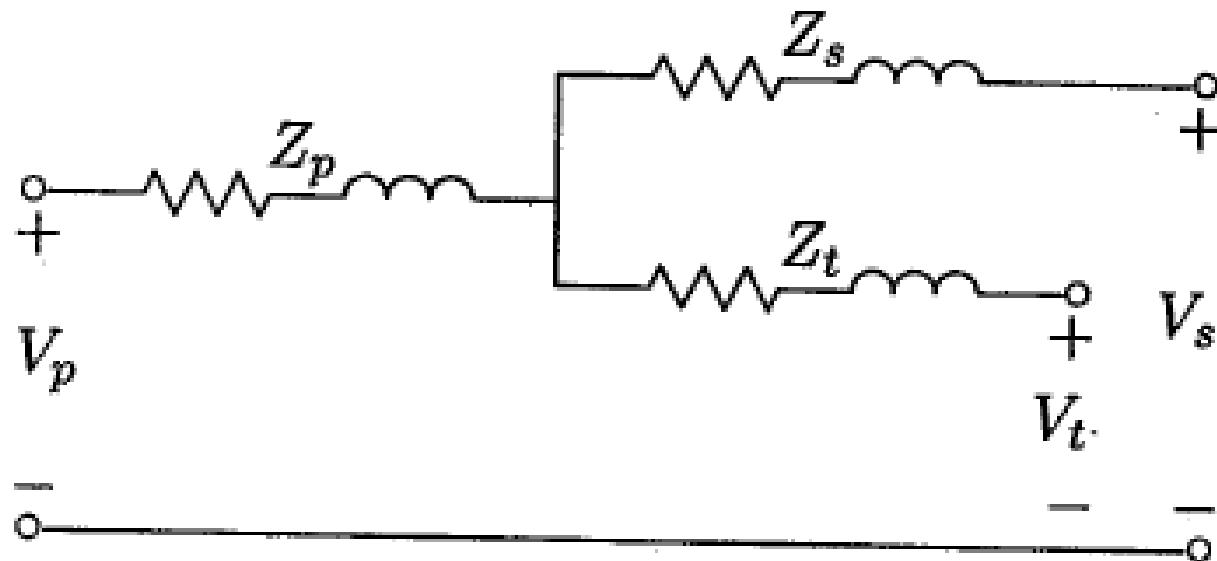

**FIGURE 3.23**

Equivalent circuit of three-winding transformer.

$Z_{ps}$  = impedance measured in the primary circuit with the secondary short-circuited and the tertiary open.

$Z_{pt}$  = impedance measured in the primary circuit with the tertiary short-circuited and the secondary open.

$Z'_{st}$  = impedance measured in the secondary circuit with the tertiary short-circuited and the primary open.

Referring  $Z'_{st}$  to the primary side, we obtain

$$Z_{st} = \left( \frac{N_p}{N_s} \right)^2 Z'_{st}$$

If  $Z_p$ ,  $Z_s$ , and  $Z_t$  are the impedances of the three separate windings referred to the primary side, then

$$\begin{aligned} Z_{ps} &= Z_p + Z_s \\ Z_{pt} &= Z_p + Z_t \\ Z_{st} &= Z_s + Z_t \end{aligned} \tag{3.68}$$

Solving the above equations, we have

$$Z_p = \frac{1}{2}(Z_{ps} + Z_{pt} - Z_{st})$$


$$Z_s = \frac{1}{2}(Z_{ps} + Z_{st} - Z_{pt})$$

$$Z_t = \frac{1}{2}(Z_{pt} + Z_{st} - Z_{ps})$$

# VOLTAGE CONTROL OF TRANSFORMERS


There are two types of tap changing transformers

- (i) Off-load tap changing transformers.
- (ii) Tap changing under load (TCUL) transformers.

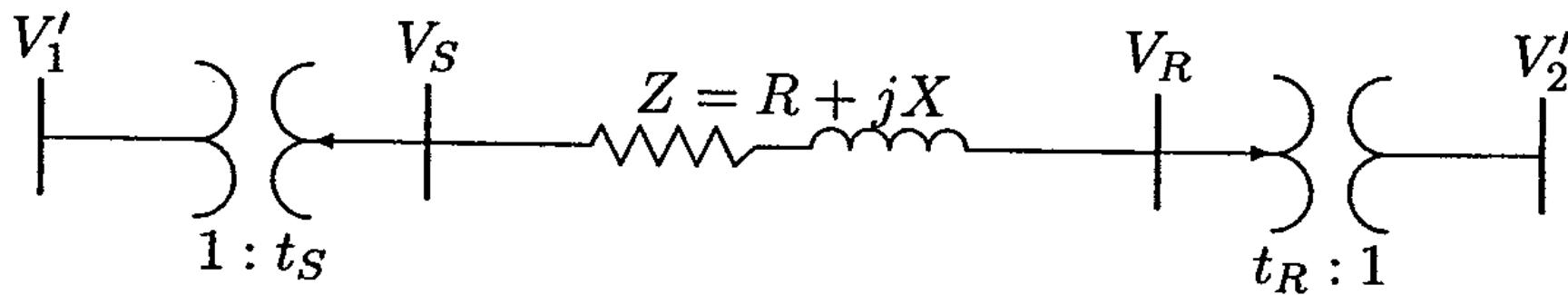

**FIGURE 3.24**

A radial line with tap changing transformers at both ends.

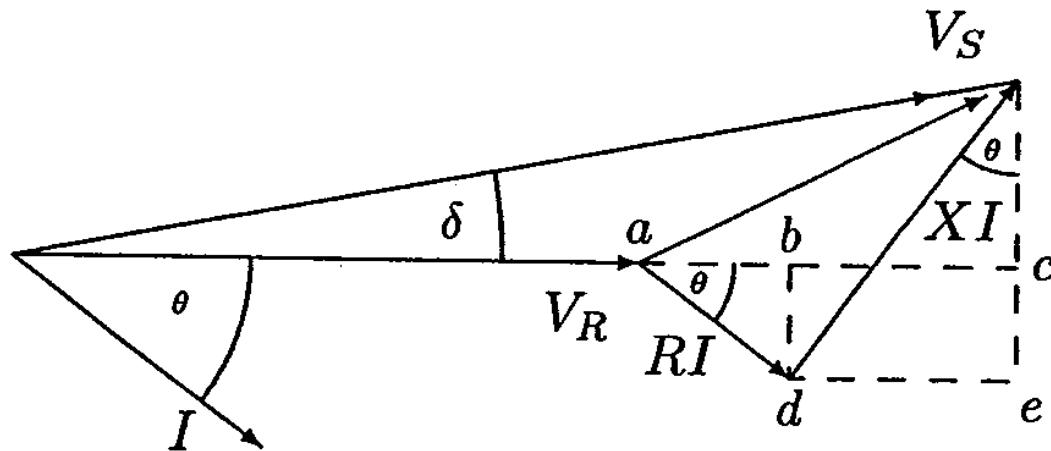

**FIGURE 3.25**  
Voltage phasor diagram.


$$V_R = V_S + (R + jX)I$$

$$t_S = \sqrt{\frac{\frac{|V'_2|}{|V'_1|}}{1 - \frac{RP_\phi + XQ_\phi}{|V'_1||V'_2|}}}$$

# MODEL TRANSMISI

- TRANSMISI PENDEK ( $< 80$  km)


$$\begin{aligned} Z &= (r + j\omega L)\ell \\ &= R + jX \end{aligned}$$

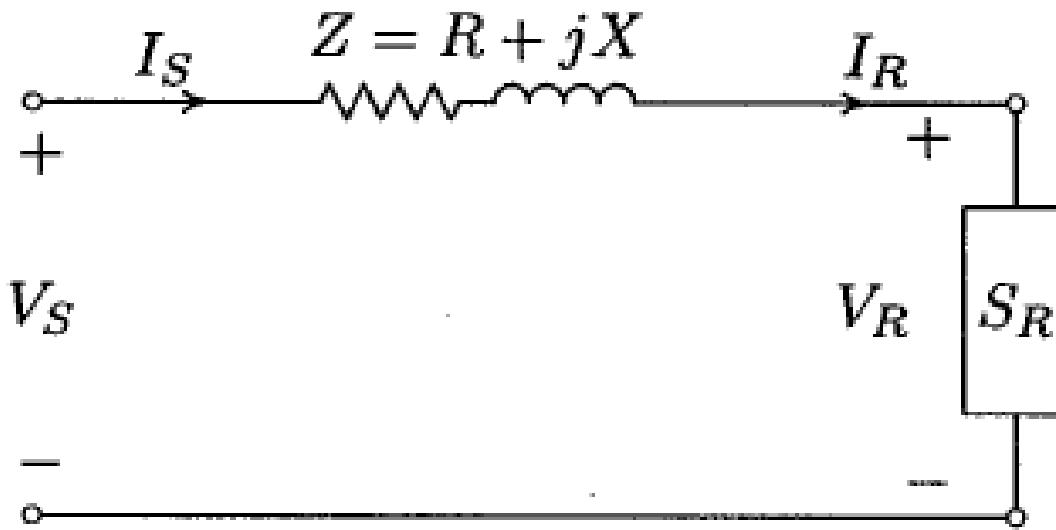

**FIGURE 5.1**  
Short line model.

$$I_R=\frac{S^*_{R(3\phi)}}{3V^*_R}$$

$$V_S=V_R+ZI_R$$

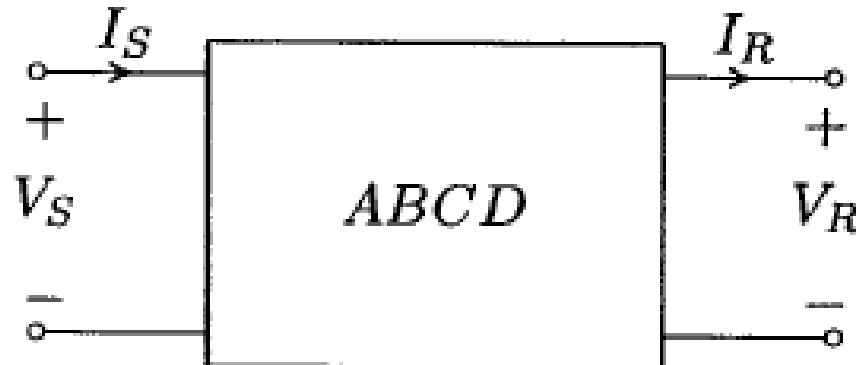

**FIGURE 5.2**

Two-port representation of a transmission line.

$$V_S = AV_R + BI_R \quad (5.5)$$


$$I_S = CV_R + DI_R \quad (5.6)$$

or in matrix form


$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \quad (5.7)$$

According to (5.3) and (5.4), for short line model

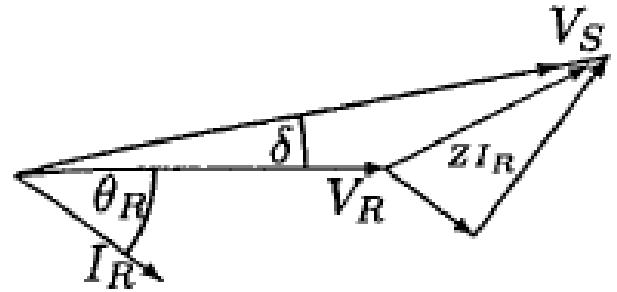
$$A = 1 \quad B = Z \quad C = 0 \quad D = 1 \quad (5.8)$$



(a) Lagging pf load

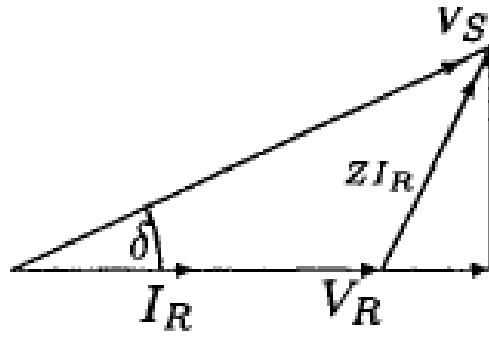

(b) Upf load

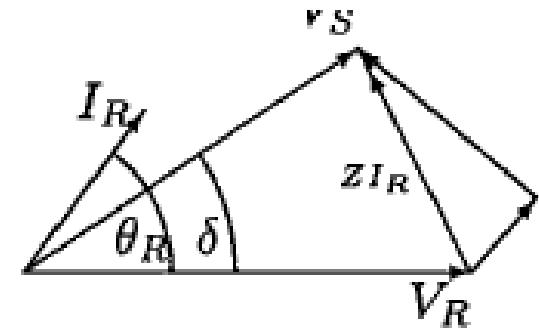


(c) Leading pf load

**FIGURE 5.3**

Phasor diagram for short line.

# TRANSMISI MENENGAH ( $80\text{km} < L < 250\text{ km}$ )

ADMITANSI SHUNT :  $Y = (g + j\omega C)\ell$

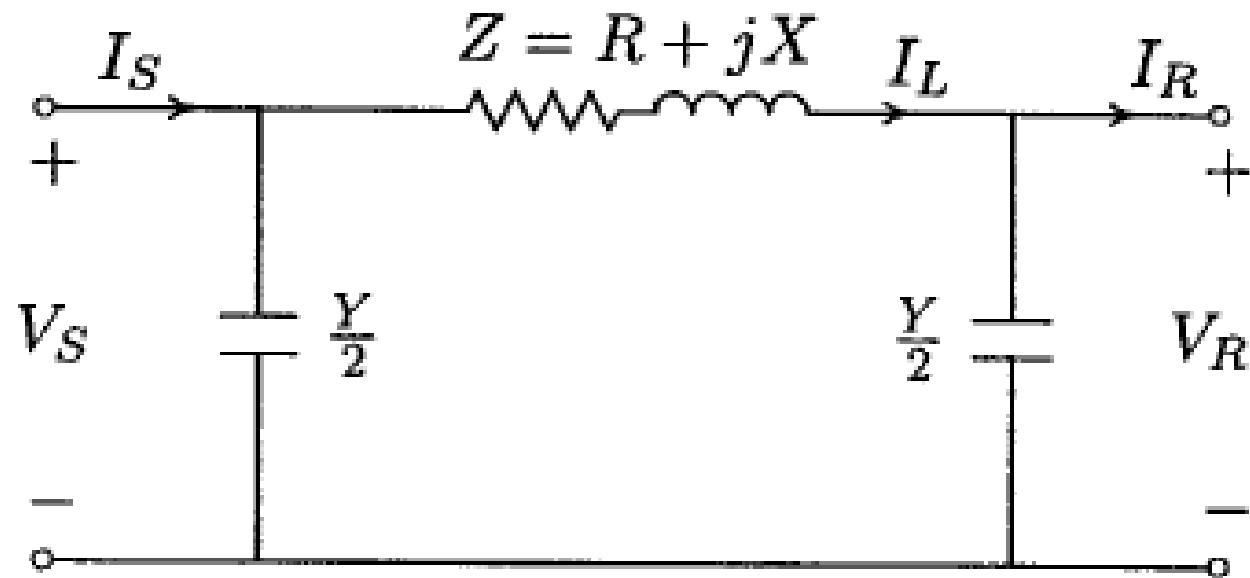

**FIGURE 5.4**

Nominal  $\pi$  model for medium length line.

From KCL the current in the series impedance designated by  $I_L$  is

$$I_L = I_R + \frac{Y}{2} V_R$$

From KVL the sending end voltage is

$$V_S = V_R + Z I_L$$

Substituting for  $I_L$  from (5.15), we obtain

$$V_S = \left(1 + \frac{ZY}{2}\right) V_R + Z I_R$$

The sending end current is

$$I_S = I_L + \frac{Y}{2} V_S$$

Substituting for  $I_L$  and  $V_S$

$$I_S = Y \left( 1 + \frac{ZY}{4} \right) V_R + \left( 1 + \frac{ZY}{2} \right) I_R \quad (5.19)$$


Comparing (5.17) and (5.19) with (5.5) and (5.6), the  $ABCD$  constants for the nominal  $\pi$  model are given by

$$A = \left( 1 + \frac{ZY}{2} \right) \quad B = Z \quad (5.20)$$

$$C = Y \left( 1 + \frac{ZY}{4} \right) \quad D = \left( 1 + \frac{ZY}{2} \right) \quad (5.21)$$


$$\begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_S \\ I_S \end{bmatrix}$$

# TRANSMISI PANJANG (>250 KM)

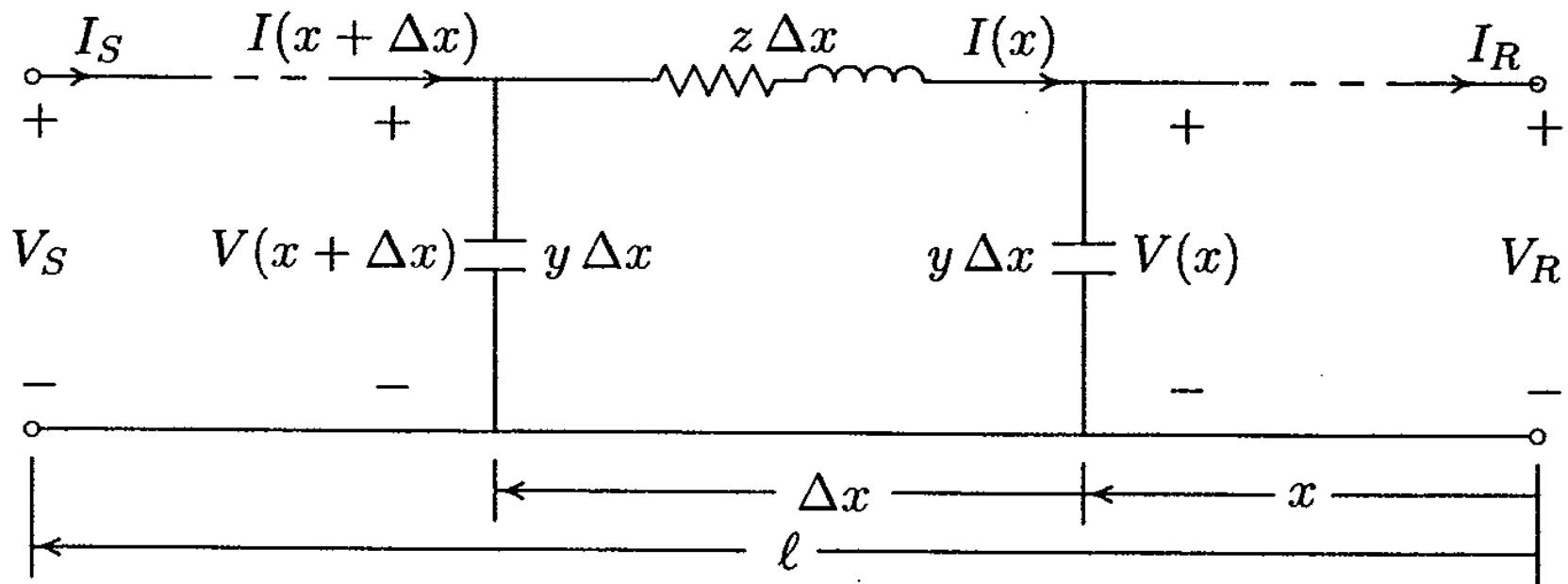

**FIGURE 5.5**

Long line with distributed parameters.

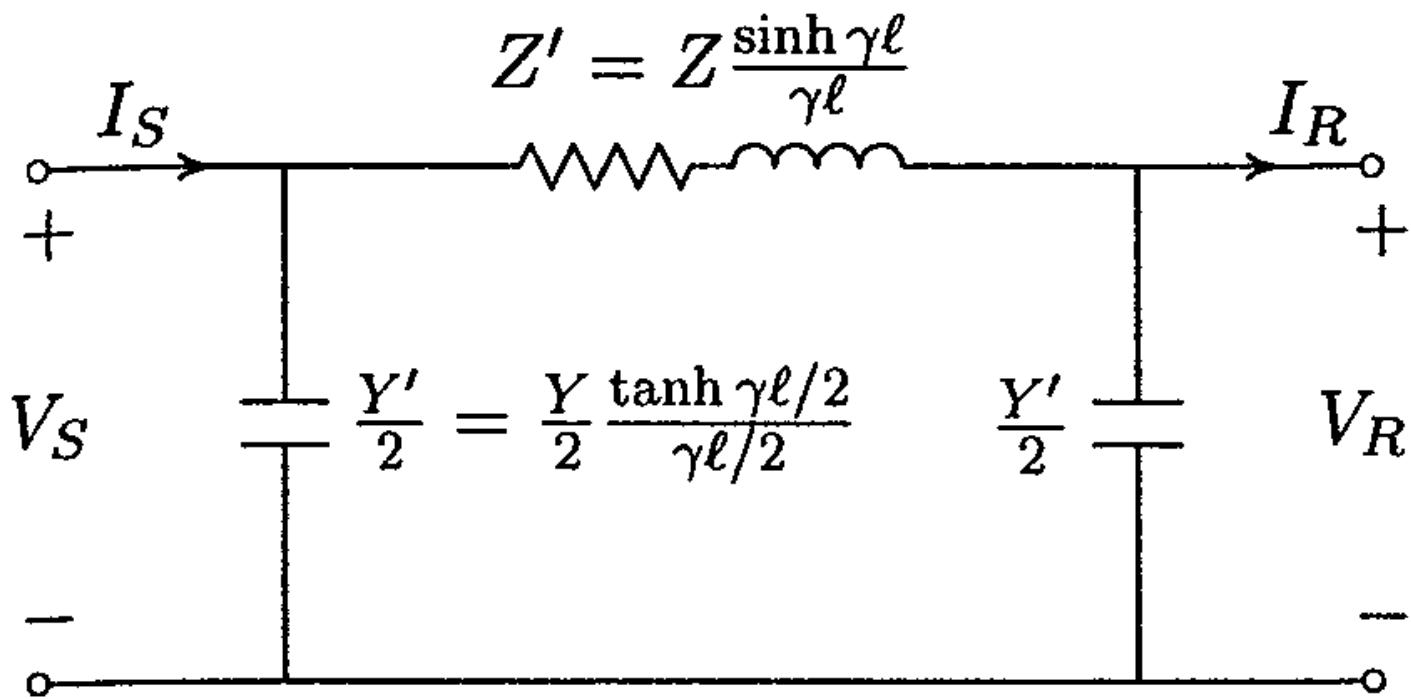

**FIGURE 5.6**

Equivalent  $\pi$  model for long length line.

$$Z' = Z_c \sinh \gamma \ell = Z \frac{\sinh \gamma \ell}{\gamma \ell}$$

$$\frac{Y'}{2} = \frac{1}{Z_c} \tanh \frac{\gamma \ell}{2} = \frac{Y}{2} \frac{\tanh \gamma \ell / 2}{\gamma \ell / 2}$$