

Menganalisa gangguan 3 phase seimbang dengan menggunakan bus impedance matrix

$$Y_{\text{bus}}\mathbf{E}^{(1)} = \mathbf{I}^{(1)} \quad (7.4.1)$$

where Y_{bus} is the positive-sequence bus admittance matrix, $\mathbf{E}^{(1)}$ is the vector of bus voltages, and $\mathbf{I}^{(1)}$ is the vector of current sources. The superscript (1) denotes the first circuit. Solving (7.4.1),

$$\mathbf{Z}_{\text{bus}}\mathbf{I}^{(1)} = \mathbf{E}^{(1)} \quad (7.4.2)$$

where

$$\mathbf{Z}_{\text{bus}} = \mathbf{Y}_{\text{bus}}^{-1} \quad (7.4.3)$$

\mathbf{Z}_{bus} , the inverse of \mathbf{Y}_{bus} , is called the positive-sequence *bus impedance matrix*. Both \mathbf{Z}_{bus} and \mathbf{Y}_{bus} are symmetric matrices.

Since the first circuit contains only one source, located at faulted bus n , the current source vector contains only one nonzero component, $I_n^{(1)} = -I_{Fn}''$. Also, the voltage at faulted bus n in the first circuit is $E_n^{(1)} = -V_F$. Rewriting (7.4.2),

$$\begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1n} & \cdots & Z_{1N} \\ Z_{21} & Z_{22} & \cdots & Z_{2n} & \cdots & Z_{2N} \\ \vdots & & & & & \\ Z_{n1} & Z_{n2} & \cdots & Z_{nn} & \cdots & Z_{nN} \\ \vdots & & & & & \\ Z_{N1} & Z_{N2} & \cdots & Z_{Nn} & \cdots & Z_{NN} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ -I_{Fn}'' \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} E_1^{(1)} \\ E_2^{(1)} \\ \vdots \\ -V_F \\ \vdots \\ E_N^{(1)} \end{bmatrix} \quad (7.4.4)$$

The minus sign associated with the current source in (7.4.4) indicates that the current injected into bus n is the negative of I_{Fn}'' , since I_{Fn}'' flows away from bus n to the neutral. From (7.4.4), the subtransient fault current is

$$I_{Fn}'' = \frac{V_F}{Z_{nn}} \quad (7.4.5)$$

Also from (7.4.4) and (7.4.5), the voltage at any bus k in the first circuit is

$$E_k^{(1)} = Z_{kn}(-I_{Fn}'') = \frac{-Z_{kn}}{Z_{nn}} V_F \quad (7.4.6)$$

The second circuit represents the prefault conditions. Neglecting prefault load current, all voltages throughout the second circuit are equal to the prefault voltage; that is, $E_k^{(2)} = V_F$ for each bus k . Applying superposition,


$$\begin{aligned}
 E_k &= E_k^{(1)} + E_k^{(2)} = \frac{-Z_{kn}}{Z_{nn}} V_F + V_F \\
 &= \left(1 - \frac{Z_{kn}}{Z_{nn}}\right) V_F \quad k = 1, 2, \dots, N
 \end{aligned} \tag{7.4.7}$$

EXAMPLE 7.4 Using Z_{bus} to compute three-phase short-circuit currents in a power system

Faults at bus 1 and 2 in Figure 7.3 are of interest. The prefault voltage is 1.05 per unit and prefault load current is neglected. (a) Determine the 2×2 positive-sequence bus impedance matrix. (b) For a bolted three-phase short circuit at bus 1, use Z_{bus} to calculate the subtransient fault current and the contribution to the fault current from the transmission line. (c) Repeat part (b) for a bolted three-phase short circuit at bus 2.

FIGURE 7.5

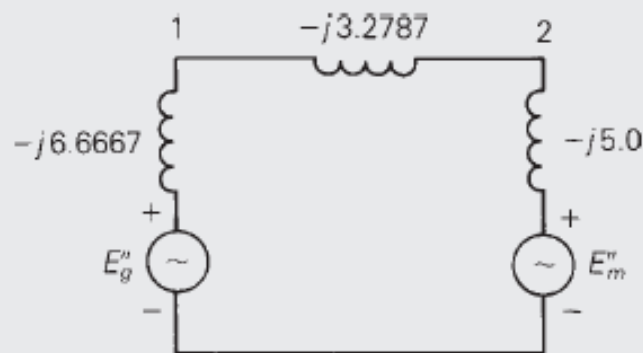Circuit of Figure 7.4(a) showing per-unit admittance values



SOLUTION

- a. The circuit of Figure 7.4(a) is redrawn in Figure 7.5 showing per-unit admittance rather than per-unit impedance values. Neglecting prefault load current, $E'_g = E''_m = V_F = 1.05/0^\circ$ per unit. From Figure 7.5, the positive-sequence bus admittance matrix is

$$\mathbf{Y}_{\text{bus}} = -j \begin{bmatrix} 9.9454 & -3.2787 \\ -3.2787 & 8.2787 \end{bmatrix} \text{ per unit}$$

Inverting \mathbf{Y}_{bus} ,

$$\mathbf{Z}_{\text{bus}} = \mathbf{Y}_{\text{bus}}^{-1} = +j \begin{bmatrix} 0.11565 & 0.04580 \\ 0.04580 & 0.13893 \end{bmatrix} \text{ per unit}$$

b. Using (7.4.5) the subtransient fault current at bus 1 is

$$I_{F1}'' = \frac{V_F}{Z_{11}} = \frac{1.05 \angle 0^\circ}{j0.11565} = -j9.079 \quad \text{per unit}$$

which agrees with the result in Example 7.3, part (a). The voltages at buses 1 and 2 during the fault are, from (7.4.7),

$$E_1 = \left(1 - \frac{Z_{11}}{Z_{11}}\right) V_F = 0$$

$$E_2 = \left(1 - \frac{Z_{21}}{Z_{11}}\right) V_F = \left(1 - \frac{j0.04580}{j0.11565}\right) 1.05 \angle 0^\circ = 0.6342 \angle 0^\circ$$

The current to the fault from the transmission line is obtained from the voltage drop from bus 2 to 1 divided by the impedance of the line and transformers T_1 and T_2 :

$$I_{21} = \frac{E_2 - E_1}{j(X_{\text{line}} + X_{T1} + X_{T2})} = \frac{0.6342 - 0}{j0.3050} = -j2.079 \quad \text{per unit}$$

which agrees with the motor current calculated in Example 7.3, part (b), where prefault load current is neglected.

c. Using (7.4.5), the subtransient fault current at bus 2 is

$$I''_{F2} = \frac{V_F}{Z_{22}} = \frac{1.05/\underline{0^\circ}}{j0.13893} = -j7.558 \quad \text{per unit}$$

and from (7.4.7),

$$E_1 = \left(1 - \frac{Z_{12}}{Z_{22}}\right) V_F = \left(1 - \frac{j0.04580}{j0.13893}\right) 1.05/\underline{0^\circ} = 0.7039/\underline{0^\circ}$$

$$E_2 = \left(1 - \frac{Z_{22}}{Z_{22}}\right) V_F = 0$$

The current to the fault from the transmission line is

$$I_{12} = \frac{E_1 - E_2}{j(X_{\text{line}} + X_{T1} + X_{T2})} = \frac{0.7039 - 0}{j0.3050} = -j2.308 \quad \text{per unit} \quad \blacksquare$$

ALGORITHM FOR BUILDING Z_{BUS} MATRIX

Z_{BUS} building algorithm is a step-by-step procedure which proceeds branch by branch. Main advantage of this method is that, any modification of the network elements does not require complete rebuilding of Z_{BUS} -matrix. Details of Z_{BUS} formulation is given below:

8.6.1 Type-1 Modification

In this case, branch impedance Z_b is added from a new bus to the reference bus. That is a new bus is added to the network and dimension of Z_{BUS} goes up by one.

Notations: i, j – old buses
 r – reference bus
 K – new bus

Figure 8.22 shows a passive linear n -bus power system network. In Fig. 8.22, an impedance Z_b is added between new bus K and the reference bus r .

From Fig. 8.22,

$$V_K = Z_b I_K$$

$$Z_{Ki} = Z_{iK} = 0; \quad \text{for } i = 1, 2, \dots, n.$$

$$\therefore Z_{KK} = Z_b$$

Therefore,

$$Z_{BUS}^{new} = \left[\begin{array}{c|c} Z_{BUS}^{old} & \begin{matrix} 0 \\ \vdots \\ 0 \end{matrix} \\ \hline \begin{matrix} 0 & \dots & 0 \end{matrix} & Z_b \end{array} \right] \quad \dots(8.22)$$

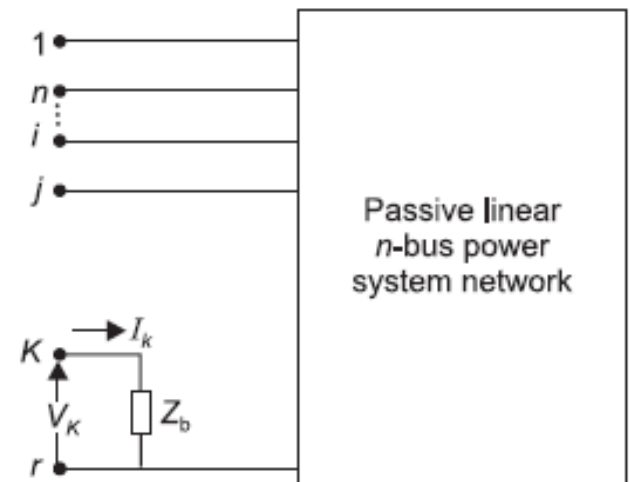


Fig. 8.22: Type-1 Modification.

where Z_{BUS}^{old} is bus impedance matrix before adding a new branch.

8.6.2 Type-2 Modification

In this case branch impedance Z_b is added from a new bus K to the old bus j as shown in Fig. 8.23.

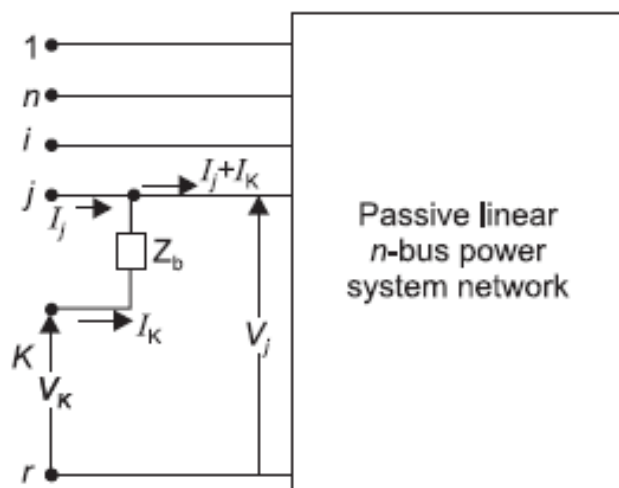


Fig. 8.23: Type-2 Modification.

From Fig. 8.23, we have

$$V_K = V_j + Z_b I_K$$

$$\therefore V_K = Z_{j1} I_1 + Z_{j2} I_2 + \dots + Z_{jj} (I_j + I_K) + \dots + Z_{jn} I_n + Z_b I_K$$

$$\therefore V_K = Z_{j1} I_1 + Z_{j2} I_2 + \dots + Z_{jj} I_j + \dots + Z_{jn} I_n + (Z_{jj} + Z_b) I_K \quad \dots(8.23)$$

Hence,

$$Z_{BUS}^{new} = \left[\begin{array}{cccc|c} & & & & Z_{1j} \\ & & & & Z_{2j} \\ & & & & \vdots \\ & & & & Z_{nj} \\ \hline Z_{j1} & Z_{j2} & \dots & Z_{jn} & Z_{jj} + Z_b \end{array} \right] \quad \dots(8.24)$$

8.6.3 Type-3 Modification

In this case, an old bus- j is connected to the reference bus- r and the impedance between these two bus is Z_b as shown in Fig. 8.24.

Referring to Fig. 8.23, if bus K is connected to reference bus r , $V_K = 0$.

Thus

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ \vdots \\ V_n \\ 0 \end{bmatrix} = \begin{bmatrix} & & & & Z_{1j} \\ & & & & Z_{2j} \\ & & & & \vdots \\ & & & & Z_{nj} \\ \hline Z_{j1} & Z_{j2} & \dots & Z_{jn} & Z_{jj} + Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \\ I_K \end{bmatrix} \quad \dots(8.25)$$

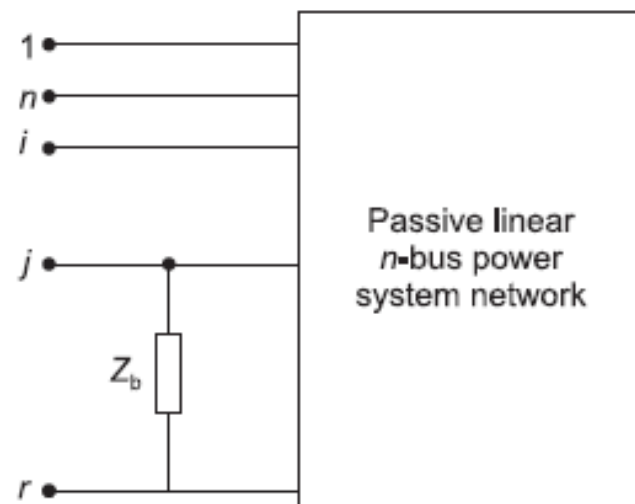


Fig. 8.24: Type-3 modification.

From equ. (8.25), we get,

$$0 = Z_{j1} I_1 + Z_{j2} I_2 + \dots + Z_{jn} I_n + (Z_{jj} + Z_b) I_K$$

$$\therefore I_K = \frac{-1}{(Z_{jj} + Z_b)} (Z_{j1} I_1 + Z_{j2} I_2 + \dots + Z_{jn} I_n) \quad \dots(8.26)$$

Expression of voltage for i -th bus can be written as:

$$V_i = Z_{i1} I_1 + Z_{i2} I_2 + \dots + Z_{in} I_n + Z_{ij} I_K \quad \dots(8.27)$$

From equations (8.27) and (8.26), we get

$$\begin{aligned} \therefore V_i &= \left[Z_{i1} - \frac{Z_{ij} Z_{j1}}{Z_{jj} + Z_b} \right] I_1 + \left[Z_{i2} - \frac{Z_{ij} Z_{j2}}{Z_{jj} + Z_b} \right] I_2 \\ &+ \dots + \left[Z_{in} - \frac{Z_{ij} Z_{jn}}{Z_{jj} + Z_b} \right] I_n \end{aligned} \quad \dots(8.28)$$

By inspection, Z_{BUS}^{new} can easily be written from equation (8.28),

$$Z_{BUS}^{new} = Z_{BUS}^{old} - \frac{1}{(Z_{jj} + Z_b)} \begin{bmatrix} Z_{1j} \\ Z_{2j} \\ \vdots \\ Z_{ij} \\ \vdots \\ Z_{nj} \end{bmatrix} [Z_{j1} \ Z_{j2} \ \dots \ Z_{jn}] \quad \dots(8.29)$$

8.6.4 Type-4 Modification

In this case, two old buses are connected and impedance between these buses is Z_b as shown in Fig. 8.25.

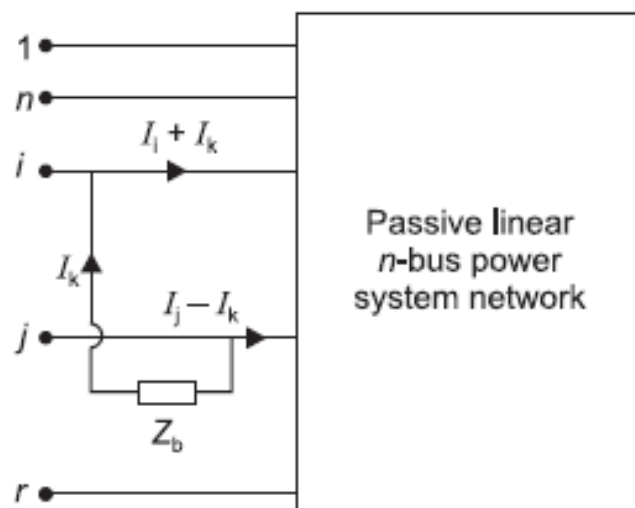


Fig. 8.25: Type-4 modification.

From Fig. 8.25, we can write,

$$V_i = Z_{i1} I_1 + Z_{i2} I_2 + \dots + Z_{ii} (I_i + I_k) + Z_{ij} (I_j - I_k) + \dots + Z_{in} I_n \quad \dots(8.30)$$

Also

$$V_j = Z_b I_k + V_i \quad \dots(8.31)$$

$$V_j = Z_{j1} I_1 + Z_{j2} I_2 + \dots + Z_{ji} (I_i + I_k) + Z_{jj} (I_j - I_k) + \dots + Z_{jn} I_n \quad \dots(8.32)$$

From equations (8.30), (8.31) and (8.32), we get

$$\begin{aligned}
 Z_{j1} I_1 + Z_{j2} I_2 + \dots + Z_{ji} (I_i + I_k) + Z_{jj} (I_j - I_k) + \dots + Z_{jn} I_n &= Z_b I_k + Z_{i1} I_1 \\
 &+ Z_{i2} I_2 + \dots + Z_{ii} (I_i + I_k) + Z_{ij} (I_j - I_k) + \dots + Z_{in} I_n \\
 \therefore 0 &= (Z_{i1} - Z_{j1}) I_1 + (Z_{i2} - Z_{j2}) I_2 + \dots + (Z_{ii} - Z_{ji}) I_i + (Z_{ij} - Z_{jj}) I_j + \dots \\
 &+ (Z_{in} - Z_{jn}) I_n + (Z_b + Z_{ii} + Z_{jj} - Z_{ij} - Z_{ji}) I_k \quad \dots(8.33)
 \end{aligned}$$

Note that $Z_{ij} = Z_{ji}$ and coefficient of I_k is $(Z_b + Z_{ii} + Z_{jj} - 2 Z_{ij})$

or

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \\ 0 \end{bmatrix} = \left[\begin{array}{ccc|c} & & & \begin{pmatrix} (Z_{i1} - Z_{j1}) \\ (Z_{i2} - Z_{j2}) \\ \vdots \\ (Z_{in} - Z_{jn}) \end{pmatrix} \\ & Z_{BUS}^{old} & & \begin{pmatrix} (Z_{i1} - Z_{j1}) \\ (Z_{i2} - Z_{j2}) \\ \vdots \\ (Z_{in} - Z_{jn}) \end{pmatrix} \\ \hline \begin{pmatrix} (Z_{i1} - Z_{j1}) \\ \dots \\ (Z_{in} - Z_{jn}) \end{pmatrix} & & & \begin{pmatrix} (Z_b + Z_{ii} + Z_{jj} - 2Z_{ij}) \\ \vdots \\ (Z_b + Z_{ii} + Z_{jj} - 2Z_{ij}) \end{pmatrix} \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \\ I_K \end{bmatrix} \quad \dots(8.34)$$

Eliminating I_k in equation (8.34) and following the same procedure for Type-2 modification, we get,

$$Z_{BUS}^{new} = Z_{BUS}^{old} - \frac{1}{(Z_b + Z_{ii} + Z_{jj} - 2 Z_{ij})} \begin{bmatrix} (Z_{i1} - Z_{j1}) \\ (Z_{i2} - Z_{j2}) \\ \vdots \\ (Z_{in} - Z_{jn}) \end{bmatrix} \times \begin{bmatrix} (Z_{i1} - Z_{j1}) \\ (Z_{i2} - Z_{j2}) \\ \vdots \\ (Z_{in} - Z_{jn}) \end{bmatrix} \quad \dots (8.35)$$

With the use of above mentioned four modifications bus impedance matrix can be formulated by a step-by-step technique considering one branch at a time.

Example 8.19 Fig. 8.26 shows a three bus network. Obtain impedance matrix Z_{BUS} .

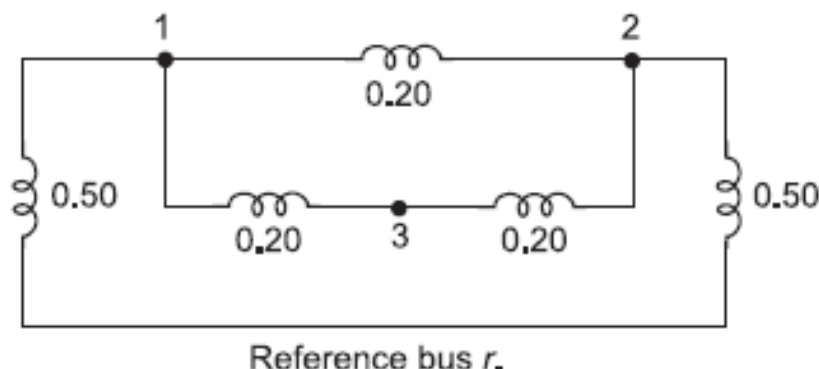


Fig. 8.26: Three bus network.

Solution:

Step-1: Add branch $Z_{1r} = 0.50$ (from new bus 1 to reference bus r)

$$\therefore Z_{BUS} = [0.50] \quad \dots (i)$$

Step-2: Type-2 modification. That is add branch $Z_{21} = 0.20$ (from new bus 2 to old bus 1)

$$\therefore Z_{BUS} = \begin{matrix} 1 \\ 2 \end{matrix} \begin{bmatrix} 0.50 & 0.50 \\ 0.50 & 0.70 \end{bmatrix} \quad \dots(ii)$$

Step-3: Add branch $Z_{13} = 0.20$ from new bus 3 to old bus 1. This is type-2 modification.

$$\therefore Z_{BUS} = \begin{bmatrix} 0.50 & 0.50 & 0.50 \\ 0.50 & 0.70 & 0.50 \\ 0.50 & 0.50 & 0.70 \end{bmatrix}$$

Step-4: Add branch Z_{2r} from old bus 2 to reference bus r . This is type-3 modification.

$$\therefore Z_{\text{BUS}} = \begin{bmatrix} 0.50 & 0.50 & 0.50 \\ 0.50 & 0.70 & 0.50 \\ 0.50 & 0.50 & 0.70 \end{bmatrix} - \frac{1}{(0.7 + 0.50)} \begin{bmatrix} 0.50 \\ 0.70 \\ 0.50 \end{bmatrix} [0.5 \quad 0.7 \quad 0.5]$$

$$\therefore Z_{\text{BUS}} = \begin{bmatrix} 0.2916 & 0.2084 & 0.2916 \\ 0.2084 & 0.2916 & 0.2084 \\ 0.2916 & 0.2084 & 0.4916 \end{bmatrix}$$

Step-5: Add branch $Z_{23} = 0.20$ from old bus 2 to old bus 3. This is type-4 modification.

$$\therefore Z_{\text{BUS}} = \begin{bmatrix} 0.2916 & 0.2084 & 0.2916 \\ 0.2084 & 0.2916 & 0.2084 \\ 0.2916 & 0.2084 & 0.4916 \end{bmatrix}$$

$$- \frac{1}{(0.20 + 0.2916 + 0.4916 - 2 \times 0.2084)} \begin{bmatrix} -0.0832 \\ 0.0832 \\ -0.2832 \end{bmatrix} [-0.0832 \quad 0.0832 \quad -0.2832]$$

$$\therefore Z_{\text{BUS}} = \begin{bmatrix} 0.2793 & 0.2206 & 0.2500 \\ 0.2206 & 0.2793 & 0.2500 \\ 0.2500 & 0.2500 & 0.3500 \end{bmatrix}$$

TUGAS 4

A single-line diagram of a four-bus system is shown in Figure 7.20, for which Z_{BUS} is given below:

$$Z_{\text{BUS}} = j \begin{bmatrix} 0.25 & 0.2 & 0.16 & 0.14 \\ 0.2 & 0.23 & 0.15 & 0.151 \\ 0.16 & 0.15 & 0.196 & 0.1 \\ 0.14 & 0.151 & 0.1 & 0.195 \end{bmatrix} \text{ per unit}$$

Let a three-phase fault occur at bus 2 of the network.

- Calculate the initial symmetrical RMS current in the fault.
- Determine the voltages during the fault at buses 1, 3, and 4.
- Compute the fault currents contributed to bus 2 by the adjacent unfaulted buses 1, 3, and 4.
- Find the current flow in the line from bus 3 to bus 1. Assume the prefault voltage V_f at bus 2 to be $1/0^\circ$ pu, and neglect all prefault currents.

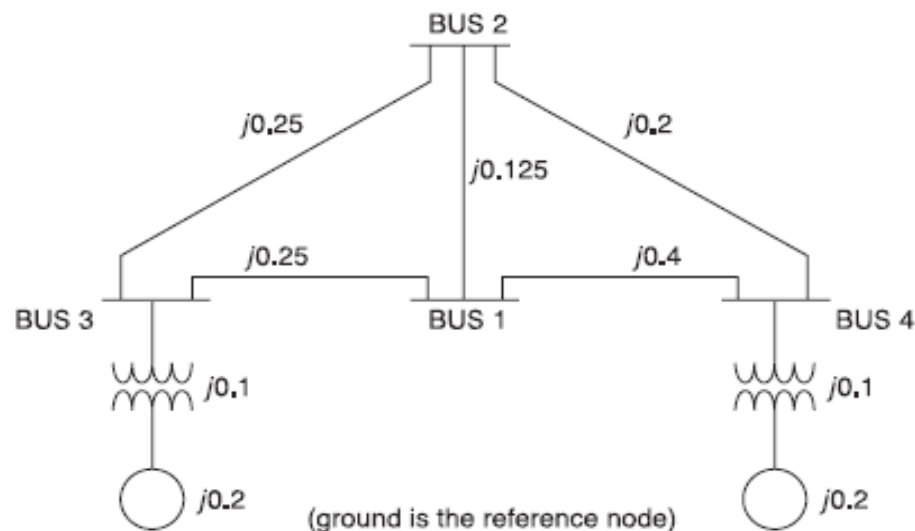


FIGURE 7.20

Single-line diagram for
Problem 7.23